

- 3.51.** In the circuit of Fig. 3.87, $R_1 = 500\ \Omega$ and $R_2 = 1\ \text{k}\Omega$. Use SPICE to construct the input/output characteristic for $-2\ \text{V} < V_{in} < +2\ \text{V}$. Also, plot the current flowing through R_1 as a function of V_{in} .

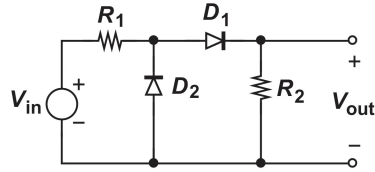


Figure 3.87

- 3.52.** The rectifier shown in Fig. 3.88 is driven by a 60-Hz sinusoid input with a peak amplitude of 5 V. Using the transient analysis in SPICE,
- Determine the peak-to-peak ripple at the output.
 - Determine the peak current flowing through D_1 .
 - Compute the heaviest load (smallest R_L) that the circuit can drive while maintaining a ripple less than $200\ \text{mV}_{pp}$.

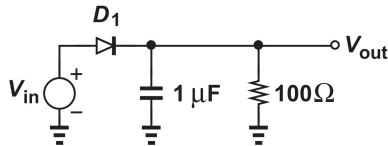


Figure 3.88

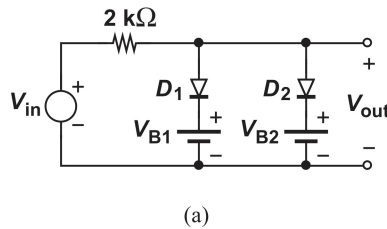


Figure 3.90

- 3.53.** The circuit of Fig. 3.89 is used in some analog circuits. Plot the input/output characteristic for $-2\ \text{V} < V_{in} < +2\ \text{V}$ and determine the maximum input range across which $|V_{in} - V_{out}| < 5\ \text{mV}$.

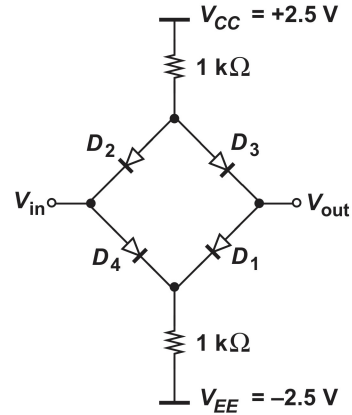


Figure 3.89

- 3.54.** The circuit shown in Fig. 3.90 can provide an approximation of a sinusoid at the output in response to a triangular input waveform. Using the dc analysis in SPICE to plot the input/output characteristic for $0 < V_{in} < 4\ \text{V}$, determine the values of V_{B1} and V_{B2} such that the characteristic closely resembles a sinusoid.

